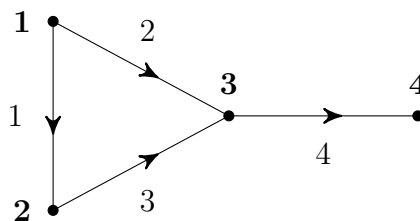


Read: Strang, Section 8.2. *Suggested short conceptual exercises: #15–18.*

Consider the graph shown below, on $n = 4$ vertices and $m = 4$ edges.



Answer the following questions. *Write clearly and concisely!* Part of your grade will be on the presentation of your solutions.

1. Write down the 4×4 incidence matrix \mathbf{A} for this graph, given the vertex and edge labels above. Compute the rank of \mathbf{A} and solve $\mathbf{A}\mathbf{x} = \mathbf{0}$, thereby finding its nullspace. The components of \mathbf{x} are the *potentials* at the vertices. Describe in a sentence what a vector \mathbf{x} in $N(\mathbf{A})$ physically represents. What type of graph would have $N(\mathbf{A})$ of dimension greater than 1?
2. Solve $\mathbf{A}^T\mathbf{y} = \mathbf{0}$ for \mathbf{y} , thereby finding the left nullspace of \mathbf{A} . Recall that $\text{rank } \mathbf{A} = \text{rank } \mathbf{A}^T$. The components of \mathbf{y} are *currents* on the edges. Describe in a sentence what a vector \mathbf{y} in $N(\mathbf{A}^T)$ physically represents.
3. Use elimination to find the ordinary echelon matrix \mathbf{U} of \mathbf{A} . What *spanning tree* corresponds to the nonzero rows of \mathbf{U} ? Sketch this tree on the network.
4. Determine the requirement(s) that the b_i 's must satisfy for $\mathbf{A}\mathbf{x} = \mathbf{b}$ to have a solution. The physical interpretation of this is *Kirchoff's voltage law* (KVL) – the components of $\mathbf{A}\mathbf{x}$ add to zero around every loop (so no voltage drop). How are the feasible \mathbf{b} 's related to your answer to Problem 2? Describe in a sentence what such a feasible \mathbf{b} physically represents, and what a vector \mathbf{x} solving $\mathbf{A}\mathbf{x} = \mathbf{b}$ represents.
5. The equation $\mathbf{A}^T\mathbf{y} = \mathbf{f}$ is *Kirchoff's current law* (KCL), and physically represents that at each vertex, flow in equals flow out (including sources). The vector $\mathbf{f} = (-1, 0, 0, 1)$ lies in $C(\mathbf{A}^T)$, and so $\mathbf{A}^T\mathbf{y} = \mathbf{f}$ has a solution. Solve for \mathbf{y} , and sketch the physical situation of the potential, current flows, and voltage sources and sink on the network.

Ohm's Law states that current is $\mathbf{y} = -\mathbf{C}\mathbf{A}\mathbf{x}$, where the \mathbf{C} is the *conductance matrix* which is diagonal where the (i, i) -entry is the conductance c_i on edge i . The relationship between potentials, currents, and voltage sources and sinks is summarized in the diagram below.

$$\begin{array}{ccc}
 \text{node potentials} & \mathbf{x} \xrightarrow{\quad \mathbf{A}^T \mathbf{C} \mathbf{A} \quad} \mathbf{A}^T \mathbf{C} \mathbf{A} \mathbf{x} = \mathbf{f} & \text{KCL} \\
 \downarrow \mathbf{A} & & \uparrow \mathbf{A}^T \\
 \text{potential differences; KVL} & \mathbf{A}\mathbf{x} \xrightarrow[\text{Ohm's law}]{\quad \mathbf{C} \quad} \mathbf{y} = \mathbf{C}\mathbf{A}\mathbf{x} & \text{(neg.) currents}
 \end{array}$$

Remark. In circuit theory (in physics and electrical engineering), current flows from higher potential to lower potential, which is why current is $\mathbf{y} = -\mathbf{C}\mathbf{A}\mathbf{x}$, rather than $\mathbf{y} = \mathbf{C}\mathbf{A}\mathbf{x}$. This artificial negative sign does not appear when this equation arises in mechanical engineering, where $\mathbf{y} = \mathbf{C}\mathbf{A}\mathbf{x}$ is called *Hooke's Law* for mass-spring systems, and \mathbf{C} is the diagonal matrix of the spring elasticities.

6. First, consider the case when all conductances are 1, so $\mathbf{C} = \mathbf{I}$, and compute $\mathbf{A}^T\mathbf{C}\mathbf{A} = \mathbf{A}^T\mathbf{A}$ (recall that it is symmetric!). Next, suppose the potentials at the nodes are given by $\mathbf{x} = (1, 0, 1, 0)$. Compute the resulting currents $\mathbf{y} = -\mathbf{C}\mathbf{A}\mathbf{x}$ and the vector \mathbf{f} of sources and sinks. Note that $\mathbf{f} = \mathbf{A}^T\mathbf{A}\mathbf{x}$, by KCL. Sketch the network and include the potentials \mathbf{x} , the currents \mathbf{y} , and the sources and sinks \mathbf{f} on the graph. Remember that at each node, flow in must equal flow out!
7. Now, suppose the conductances are $c_1 = 1$ and $c_2 = c_3 = c_4 = 2$. Moreover, let $\mathbf{f} = (1, -3, 4, -2)$ be the vector of sources and sinks. Determine the potentials at each node by solving $\mathbf{A}^T\mathbf{C}\mathbf{A}\mathbf{x} = \mathbf{f}$ for \mathbf{x} . Sketch the network and include the potentials \mathbf{x} , the currents \mathbf{y} , and the sources and sinks \mathbf{f} . Compare your answer to that of the previous problem.